

University of Illinois ECE445: Senior Design Laboratory

DC-DC Converter for EWB Wind Turbine Project



Group 3
Jeong-Ah Lee
Chris Livesay
Qing Janet Wang

April 27, 2006

Introduction

- DC-DC converter that connects a wind turbine output ranging from 40 – 70 V to charge 12 V lead-acid batteries.
- Will be used to improve a village's access to electricity from wind sources in India.



Benefits



- Impact on Education
- Impact on Health
- Other Electronic Equipments

Product Features

- Reliable and Low Cost
- Simple operation
- Provides power from previously unused energy
- High impact and large availability

Performance Requirements

- Output is user-adjustable between 12V and 15V at 10A, regulated
- Does not create radio frequency interference
- Does not drain battery when wind generator is not producing power
- Input and output protection:
 - Input over-voltage protection
 - Input and output overload protection
 - Input and output short circuit protection
 - Input and output reverse polarity protection


Wiring Schematic for Mozda Collective Windmill and Photovoltaic System

June 2005, Mozda, Gujarat, India



48 volt
1200 watt
10 ft diameter
Permanent
Magnet
Alternator
Windcharger

Solar PV Panels (12v-50watts)

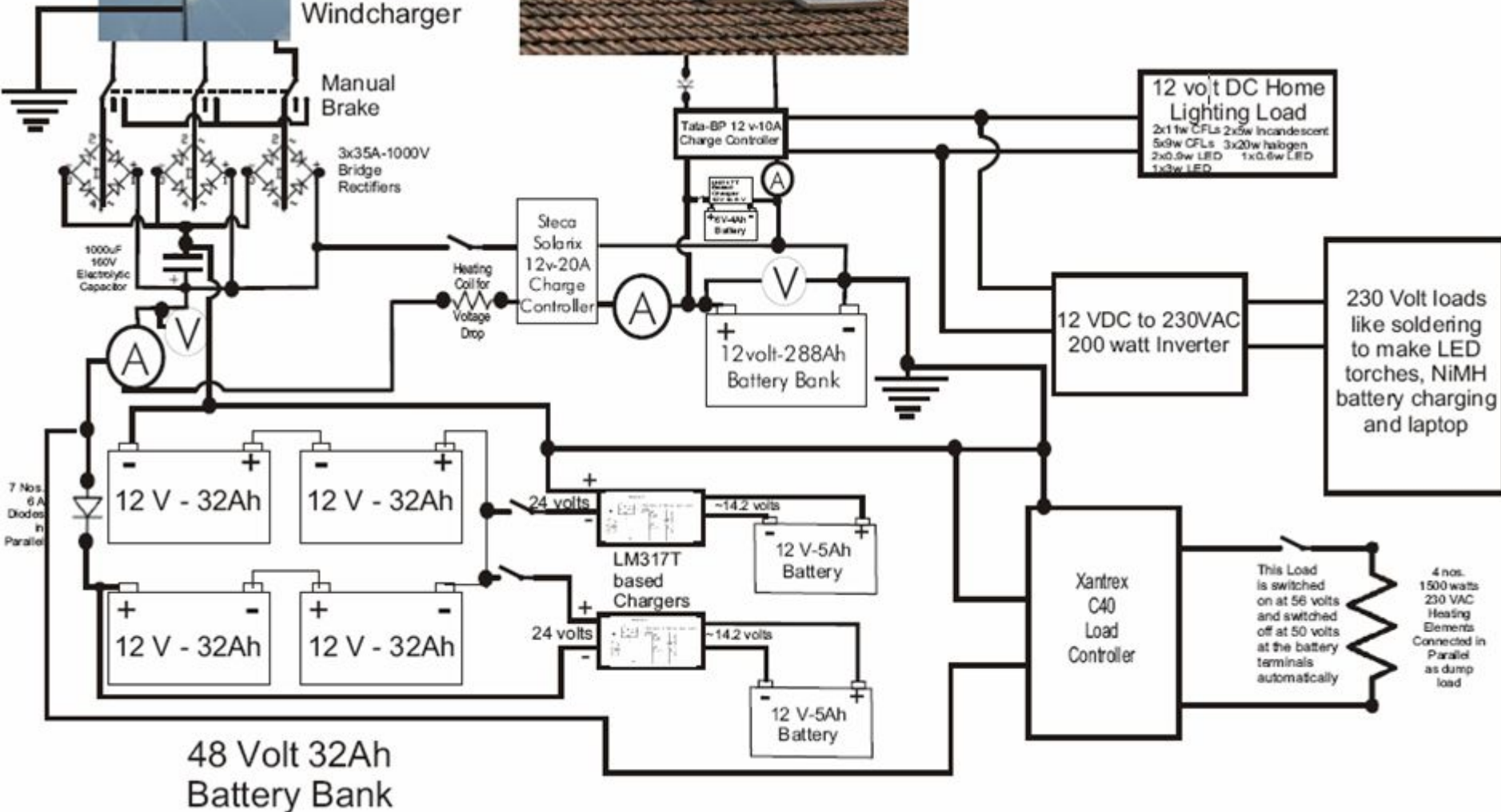

Mozda H.A.W.T. Wind Turbine

- 48 V, 1200 VA, star connected three phase ac generator [12 pole rotor, 9 coil stator]
- Maximum output voltage is around 65 V
- May exceed 125 V in case of failure (wire breakage, generator disconnection, etc.)
- Windmill Clip


Design Overview

- PWM Controller
 - To drive the converter MOSFET
- DC-DC Buck Converter
 - Input: 35 V – 85 V dc
 - Output: 12 V – 15 V dc
- Input and Output Protection
- Efficiency
 - Desire 85% efficiency

Buck vs. Flyback Converter


■ Buck Converter:

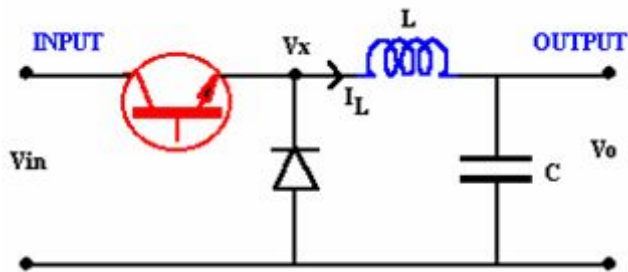- ❑ Low cost
- ❑ Least number of components
- ❑ Poor load regulation




■ Flyback Converter:

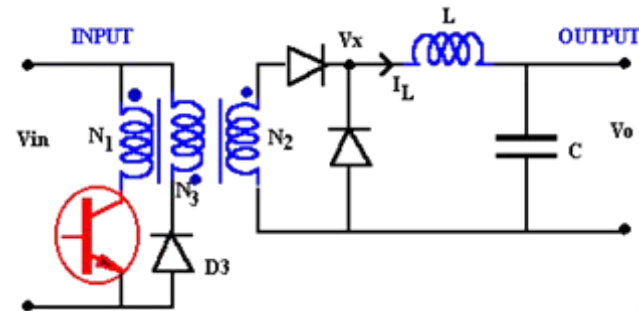
- ❑ Low output ripple and noise
- ❑ More reliable compared to buck converter, but more components



Block Diagram

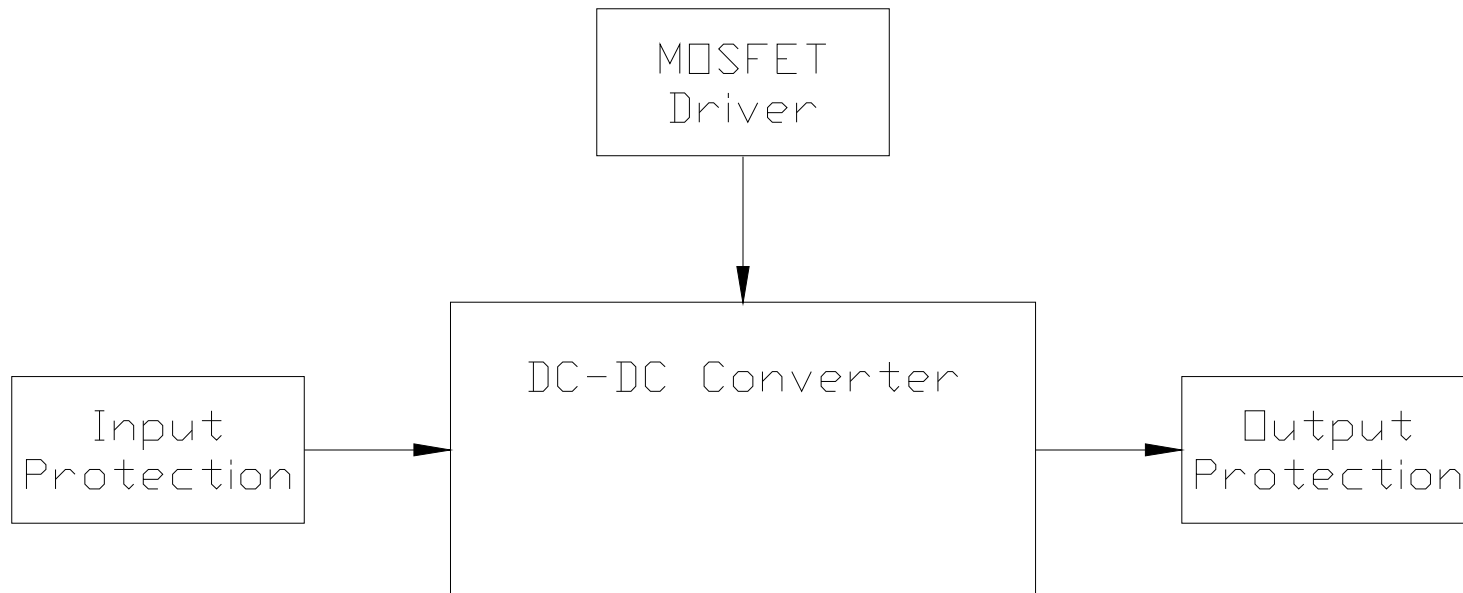

Buck Converter

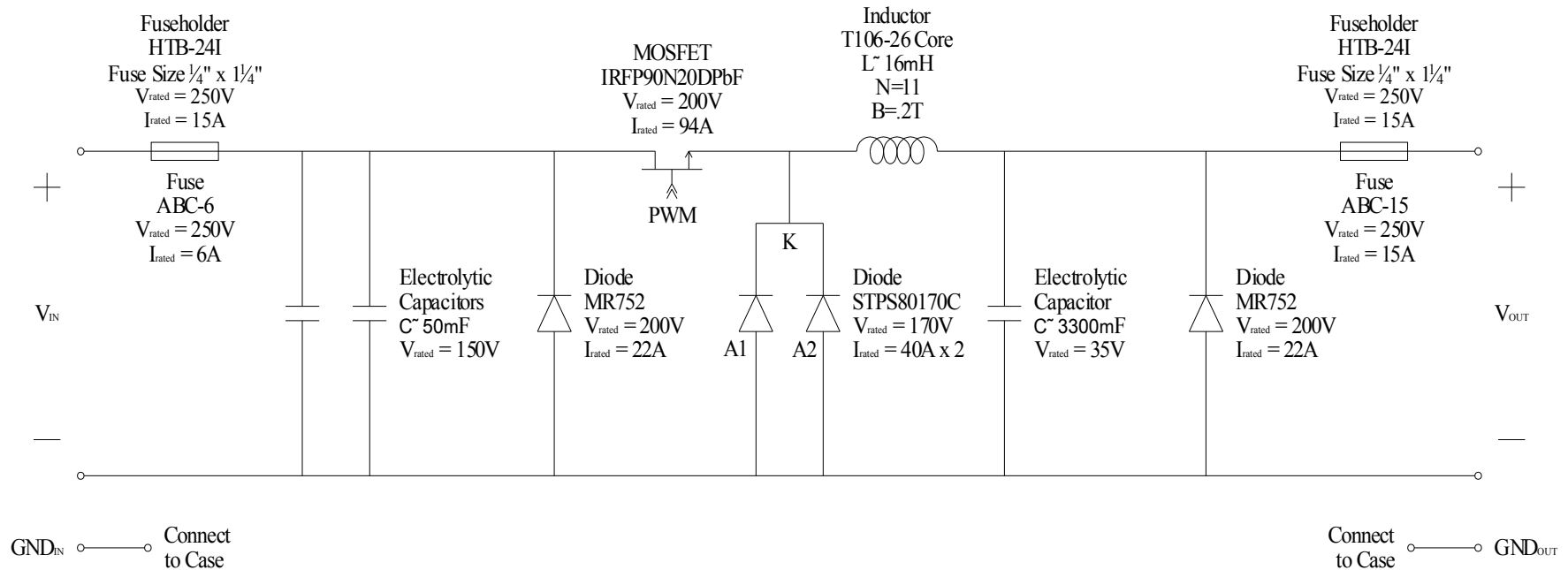

Buck Converter Components

MOSFET

- On-resistance must be low to reduce I^2R loss
- Logic-level gate drive




IRFP90N20D
TO-247AC

| V_{DSS} | $R_{DS(on) \max}$ | I_D |
|-----------|-------------------|------------------|
| 200V | 0.023 Ω | 94A [®] |

Diode

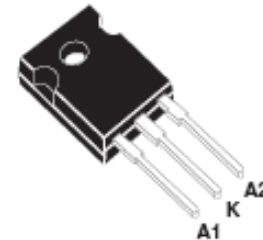- Must be a Schottky diode (quick on/off time)
- Low forward voltage drop



TO-247
STPS80170CW

| | |
|------------|----------|
| $I_F(AV)$ | 2 x 40 A |
| V_{RRM} | 170 V |
| T_j | 175 °C |
| $V_F(max)$ | 0.74 V |

Inductor Design

When selecting an inductor for a Buck converter, as with all switching regulators, you will need to define or calculate the following parameters:

- Maximum input voltage = 85V
- Output voltage = 15V
- Designed switching frequency = 100 kHz
- Maximum ripple current

$$D = \frac{V_{OUT}}{V_{IN}}$$

$$\frac{12}{85} < D < \frac{15}{35}$$

$$\boxed{.141 < D < .429}$$

$$B_{\max} = \frac{\mu * N * I_{OUT}}{l}$$

$$B_{\max} = \frac{75 * \mu_o * 11 * 10}{.0649}$$

$$\boxed{B_{\max} = .160T}$$

$$L_{CRIT} = \frac{R_{OUT} * T}{2} (1 - D)$$

$$L_{CRIT} = \frac{R_{OUT}}{2 * f} (1 - D)$$

$$L_{CRIT} = \frac{1.5}{2 * 100000} (1 - .141)$$

$$L_{CRIT} = 6.443 \mu F$$

$$\boxed{L = 10 \mu F}$$

$$N = \sqrt{\frac{L * l}{\mu * A}}$$

$$N = \sqrt{\frac{10 * 10^{-6} * .0649}{75 * \mu_o * .000066}}$$

$$\boxed{N = 11}$$

Output Filter Capacitor

- Limits the output voltage ripple
- Equivalent Series Resistance (ESR) should be kept low to reduce I^2R loss
- Aluminum Electrolytic: Low cost and high capacitance in a small package
- Design target: $\Delta v = \pm 0.5\%$
- Calculation:

$$C = I_{OUT} * \frac{D}{\Delta V * f_{SW}}$$


$$C = \frac{.429}{.01 * 1.5 * 100000}$$

$$C > 286 \mu F$$

Simulation & Waveforms

- In order to verify the overall design PSPICE was used to simulate the Buck Converter with a switch acting as the MOSFET driver


- Circuit Diagram

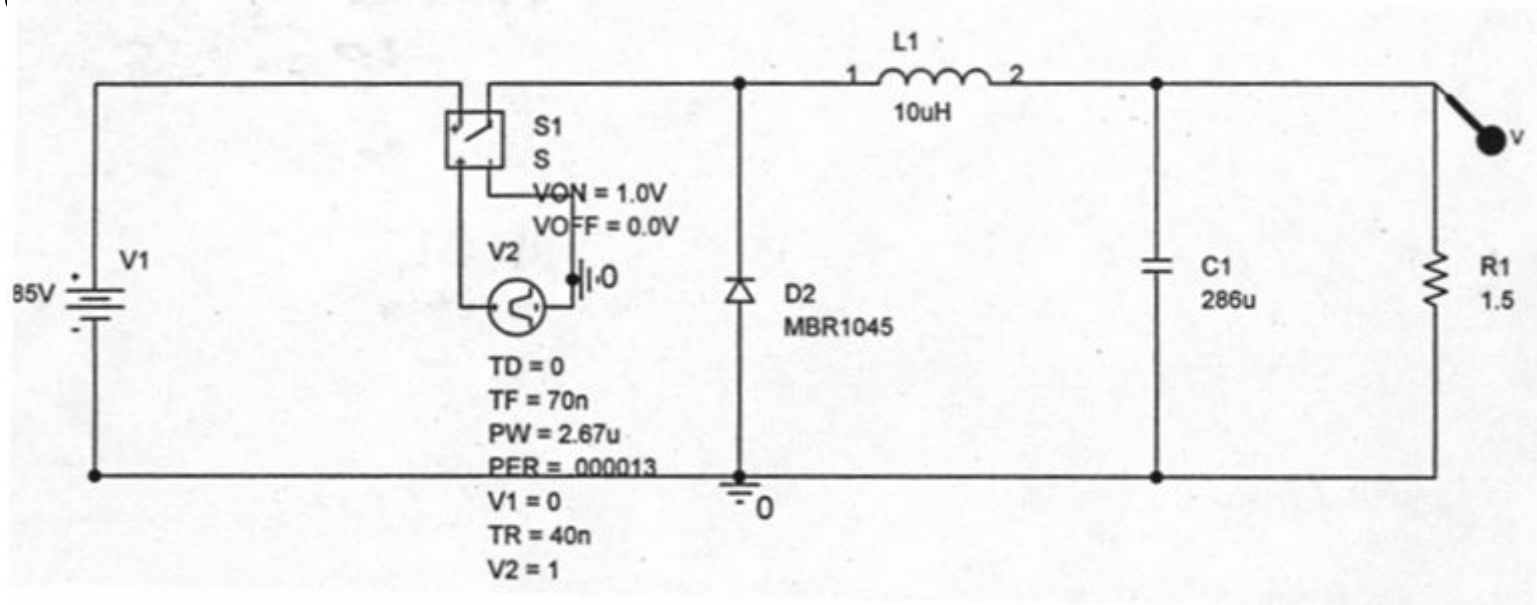


Simulation & Waveforms

- The duty ratio was adjusted accordingly to achieve the desired output voltage.

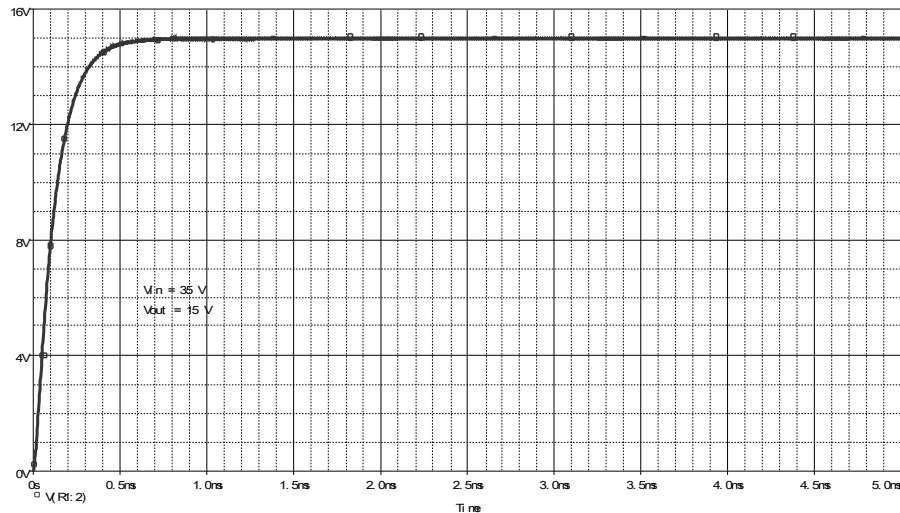
$V_{in} = 35 \text{ V}$; $V_{out} = 15 \text{ V}$; $D=0.612$



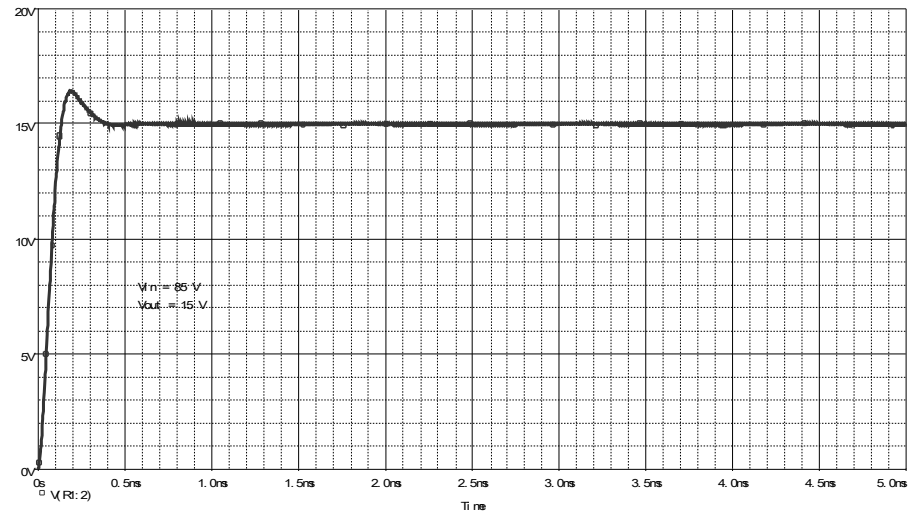
$V_{in} = 85 \text{ V}$; $V_{out} = 15 \text{ V}$; $D=0.205$



PWM Control Circuit

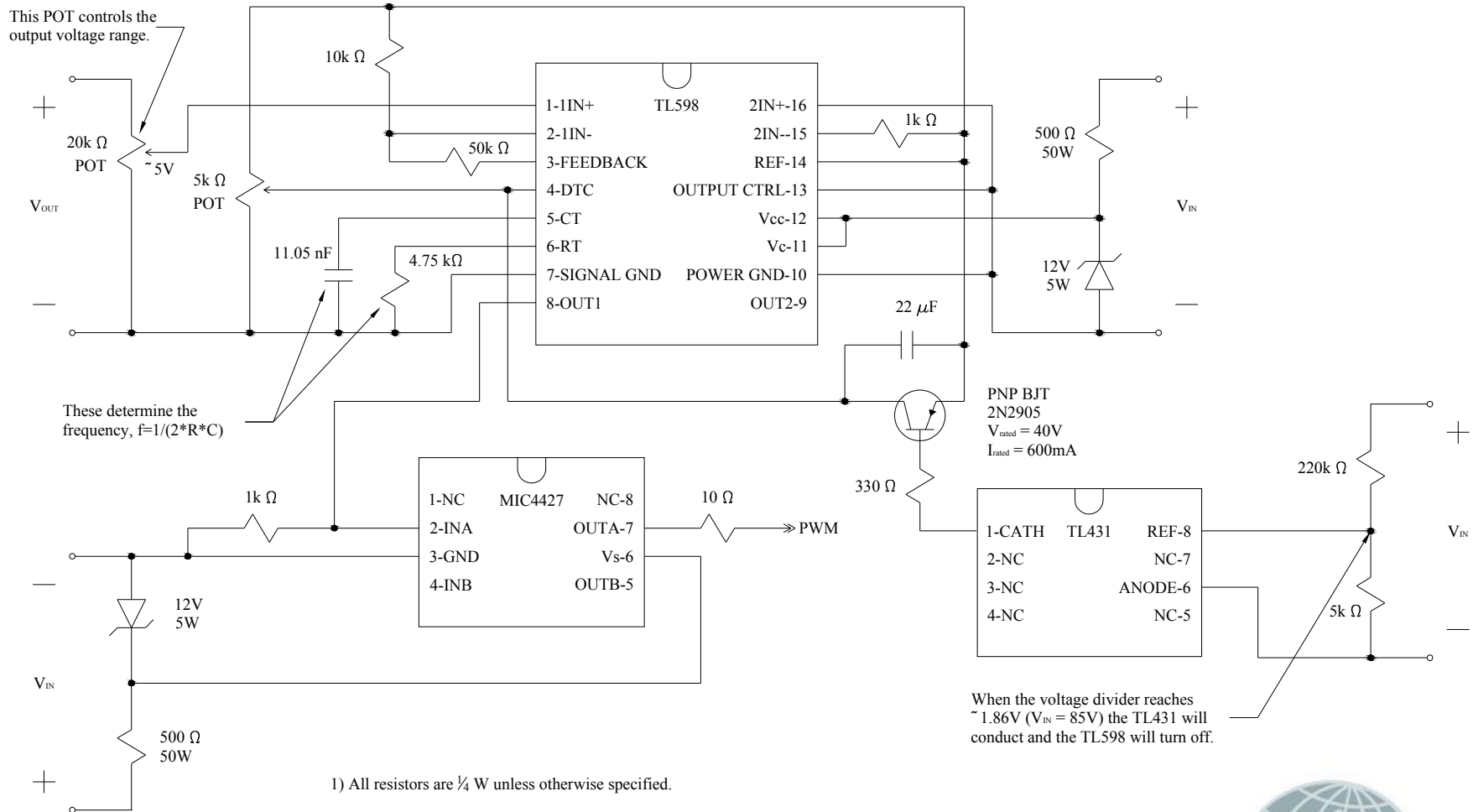

The DC-DC Converter

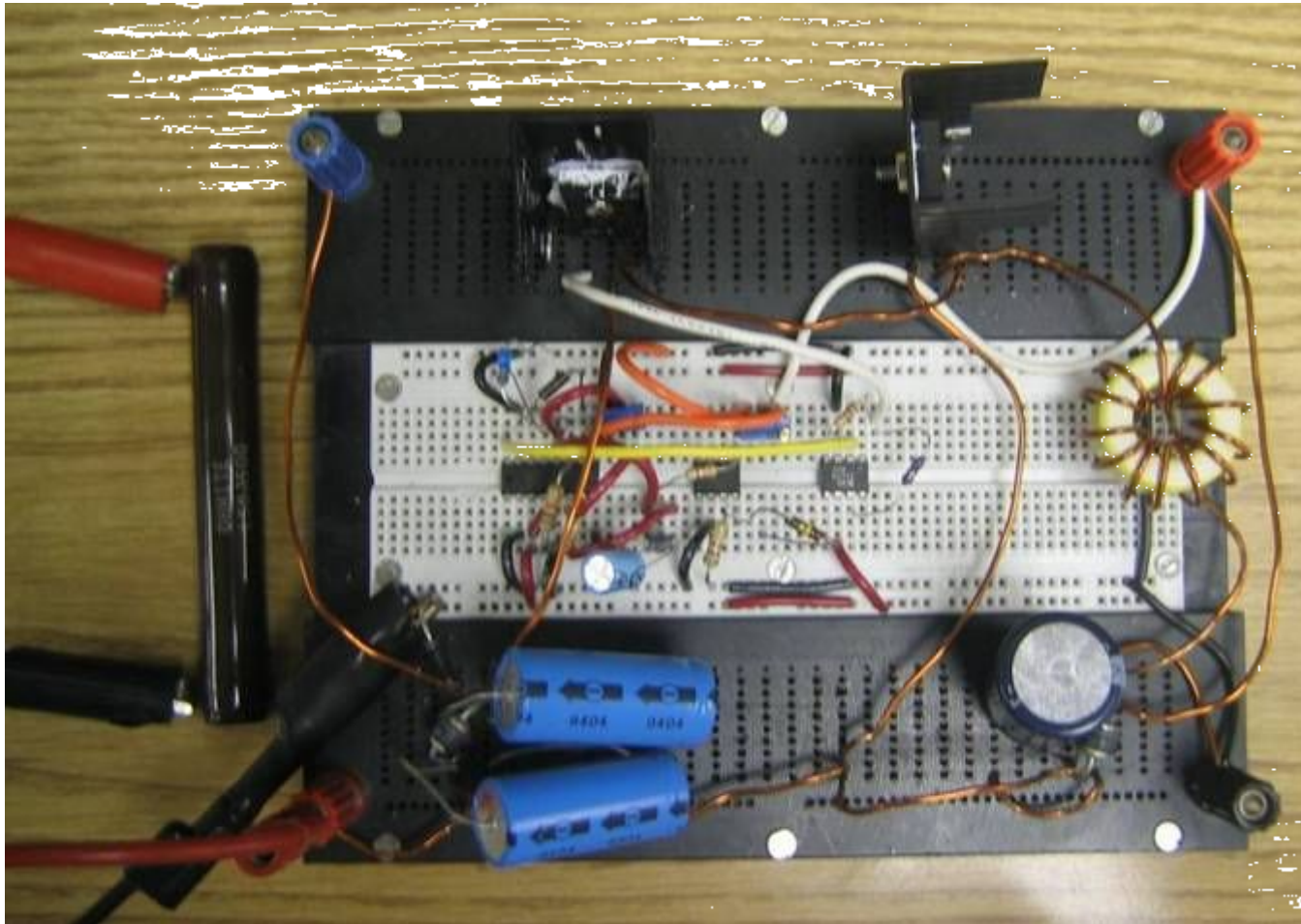


University of Illinois ECE445: Senior Design Project




Testing – Output Voltage Ripple

Voltage Ripple Test Data

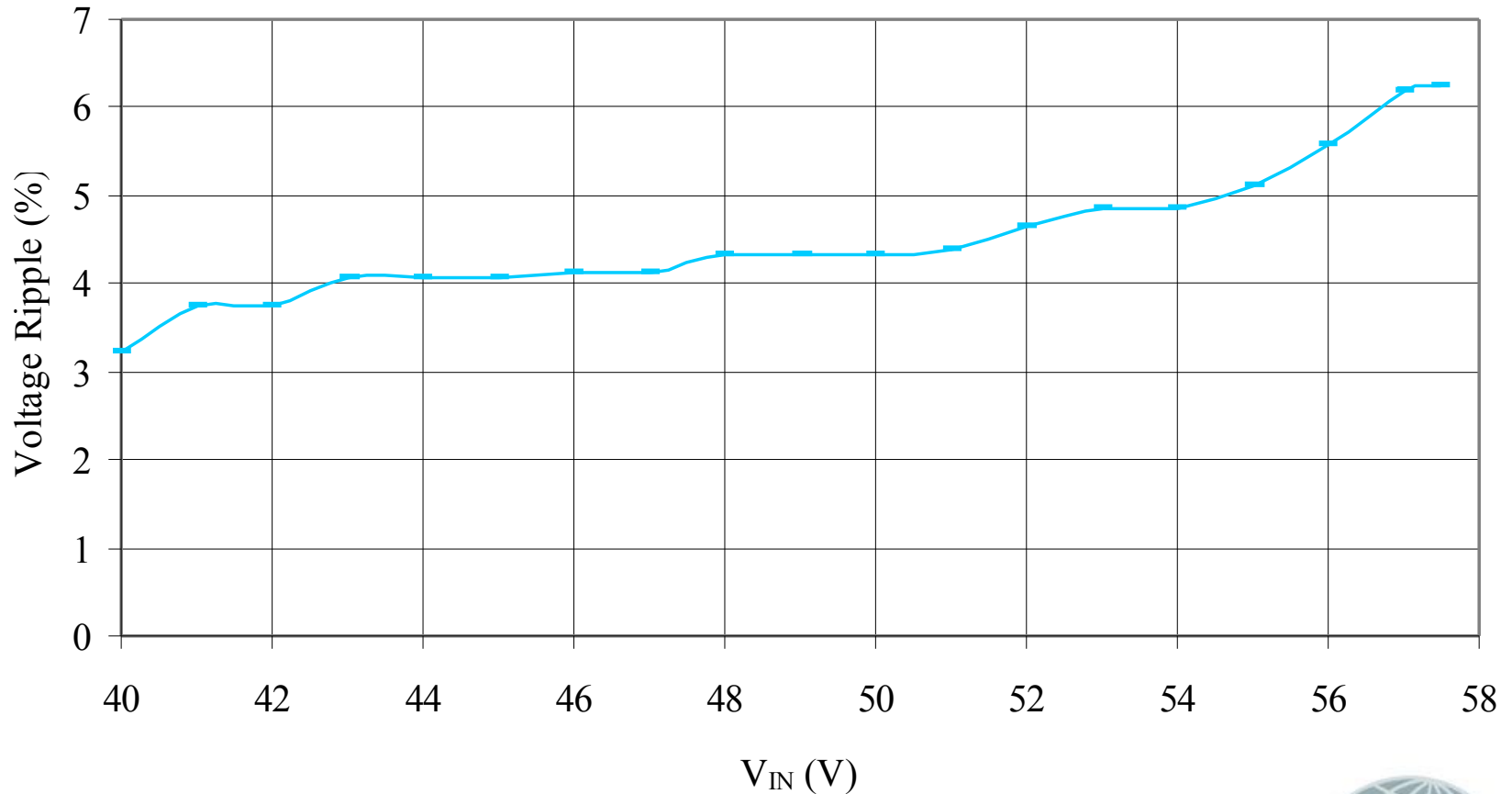

Testing – Output Voltage Ripple


- $V_{in} = 48\text{ V}$

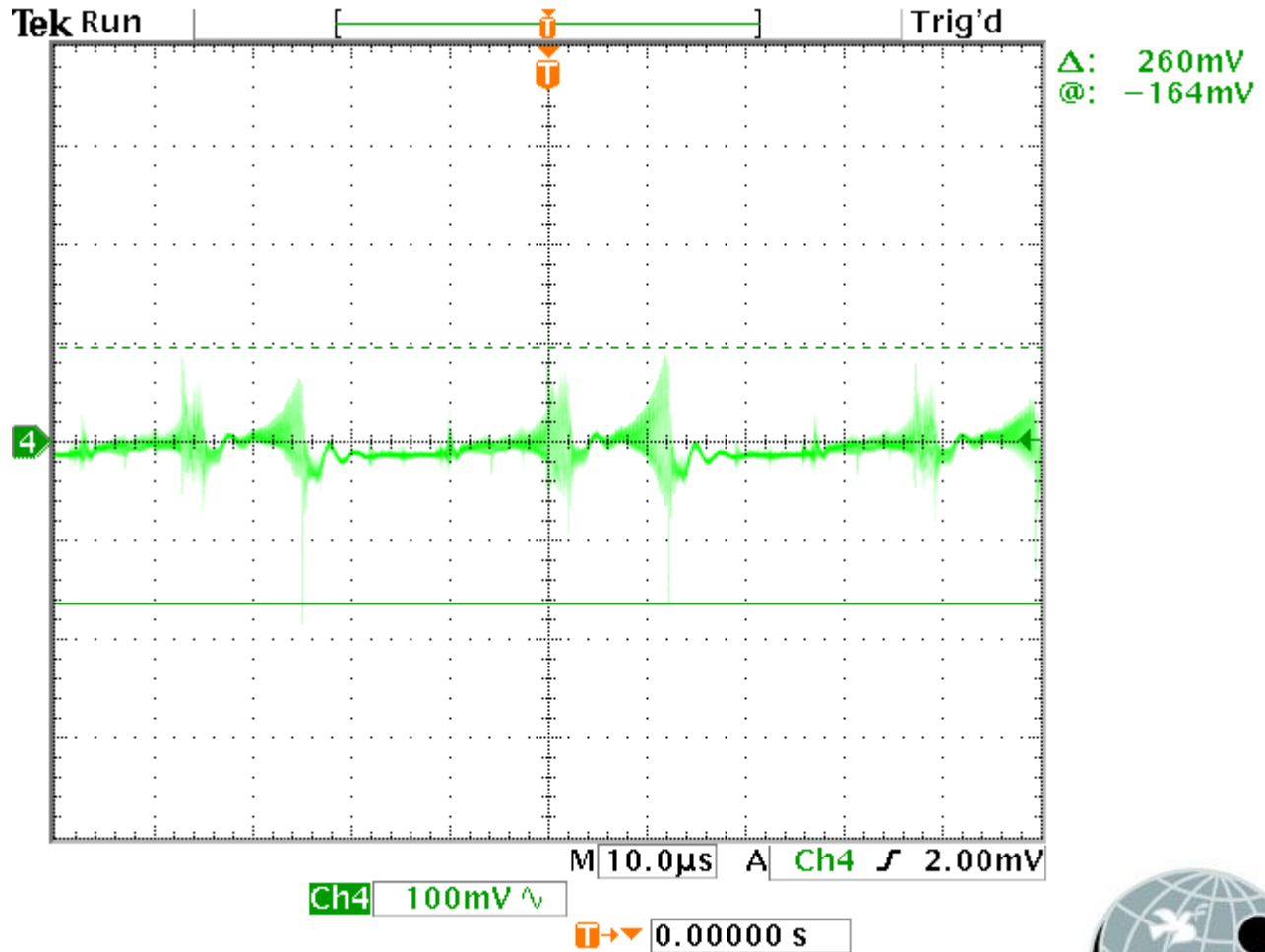


Testing - Temperature

MOSFET Test Data

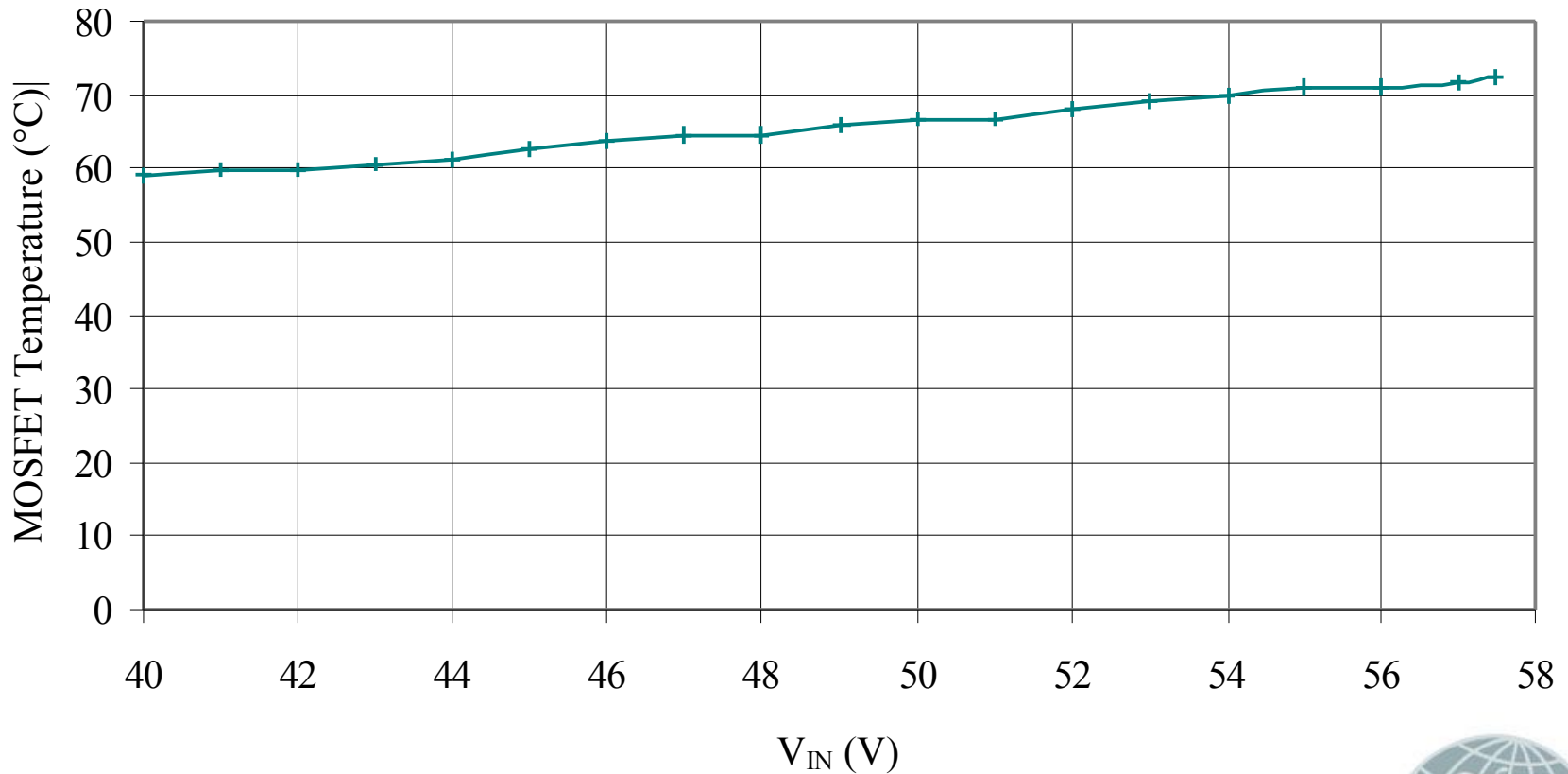
($T_{\text{Ambient}} = 23.35\text{ }^{\circ}\text{C}$)



MOSFET Gate Signal

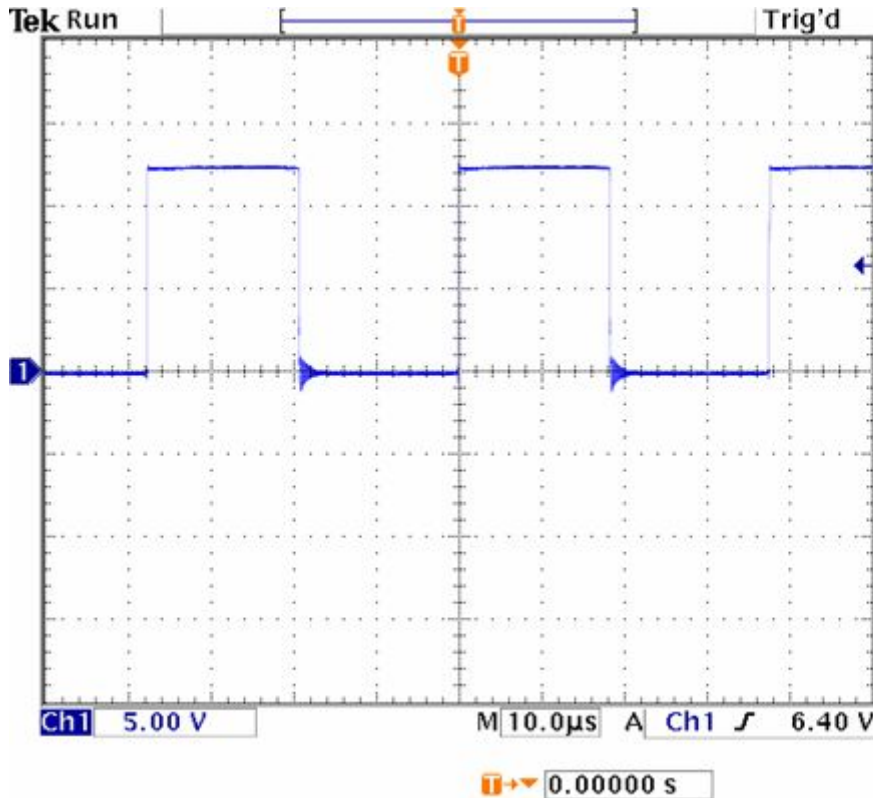


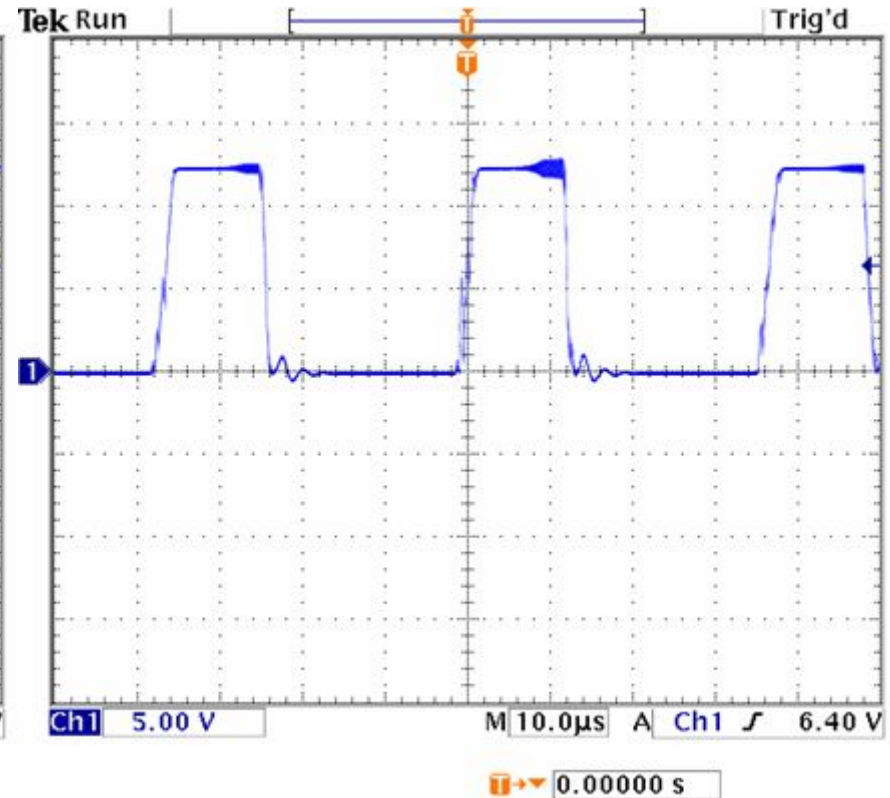When not connected to MOSFET
 $V_{in} = 48 \text{ V}$




When connected to MOSFET
 $V_{in} = 48 \text{ V}$

Results

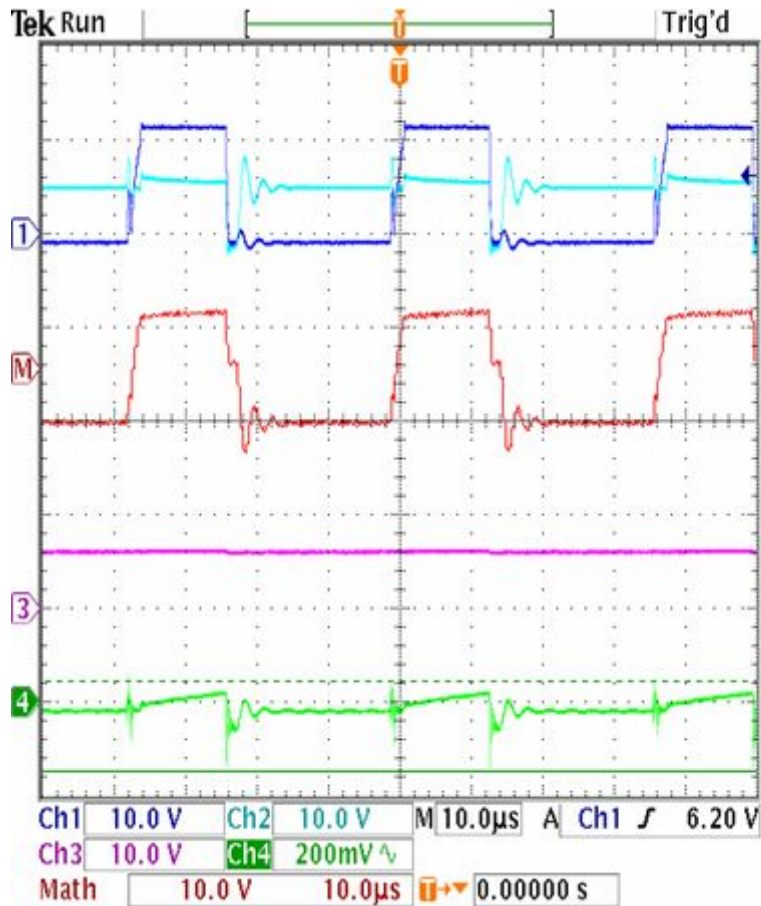


Ch1: Gate Voltage
Math: Gate-Source Voltage
Ch3: Output Voltage
Ch4: Output Ripple Voltage

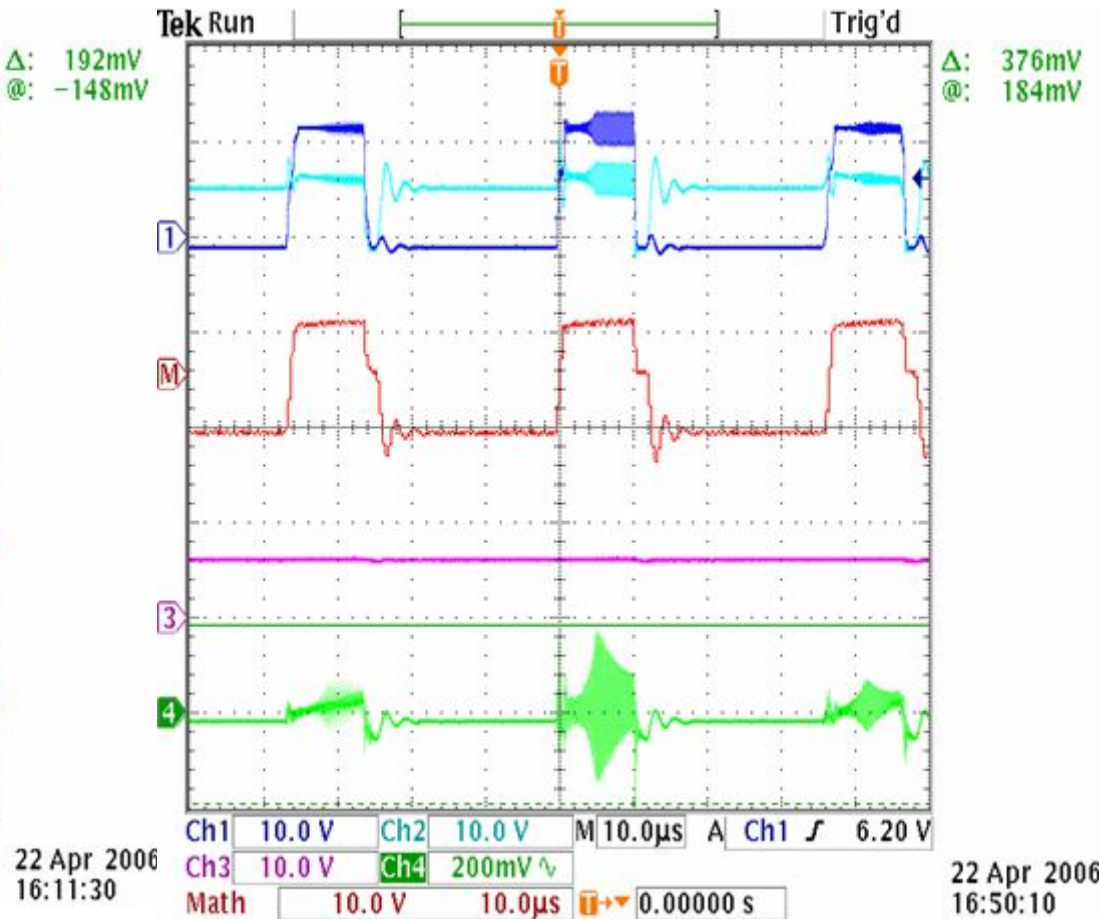

Ch2: Source Voltage
Ch3: Output Voltage

Efficiency vs. V_{IN}

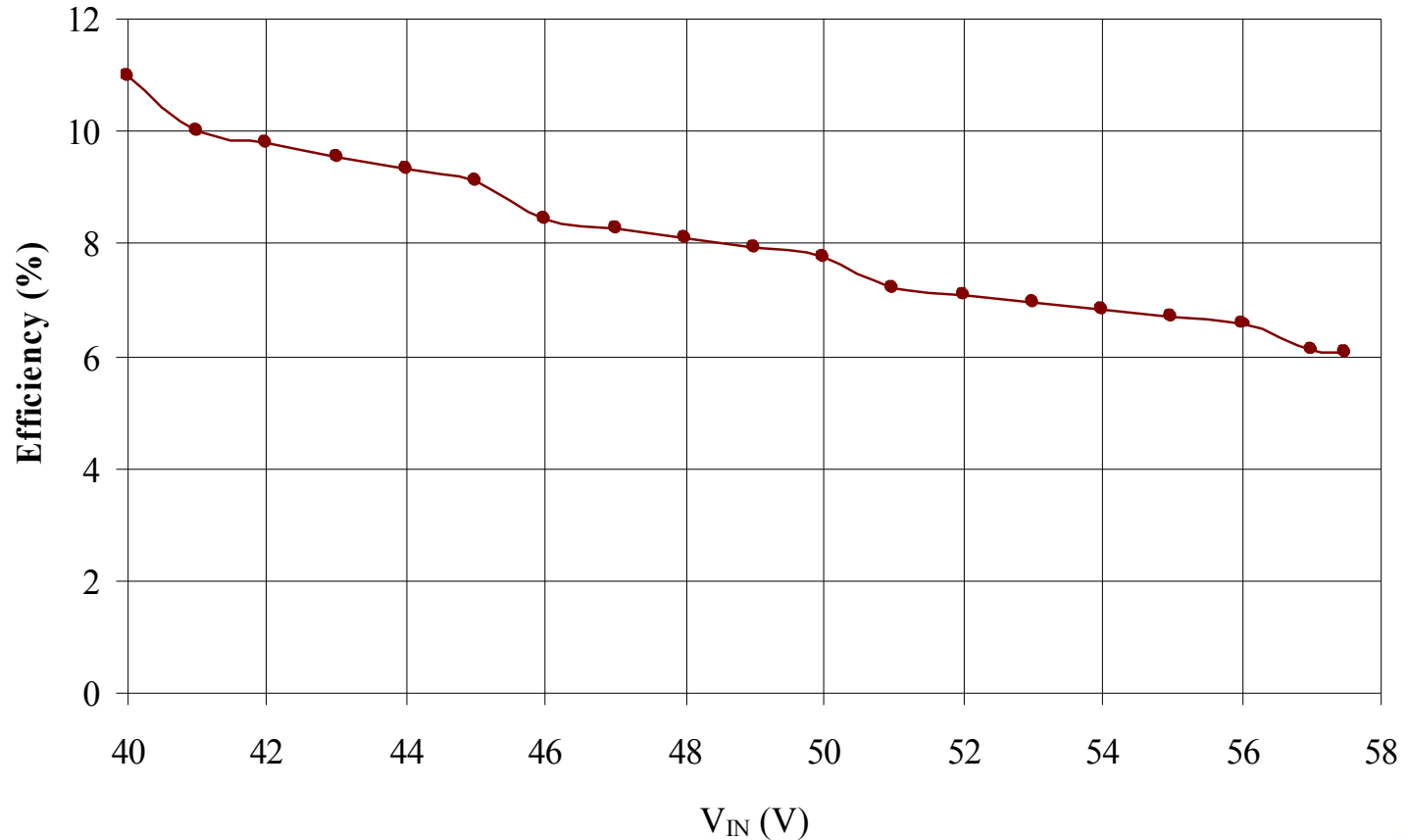

Challenges

- MOSFET heating
- Low efficiency
 - Conduction Losses
 - MOSFET on-resistance
 - Voltage drop across diode
 - Control Circuit Power Consumption
 - Switching Losses

Successes & Summary

- Our converter works.
- But only at low power.
- We met input and output protection specifications.
- Obtained a maximum of 11% efficiency on bread board.
- Recommendations:
 - Research MOSFETs more.
 - Different control chips.

Credits

- Professor Jonathan W. Kimball
- Professor Patrick Chapman
- Professor P. Scott Carney
- Michael Mazgaonkar - EWB India, Gujarat
- Austin Kirchhoff



Thank You



University of Illinois ECE445: Senior Design Project

